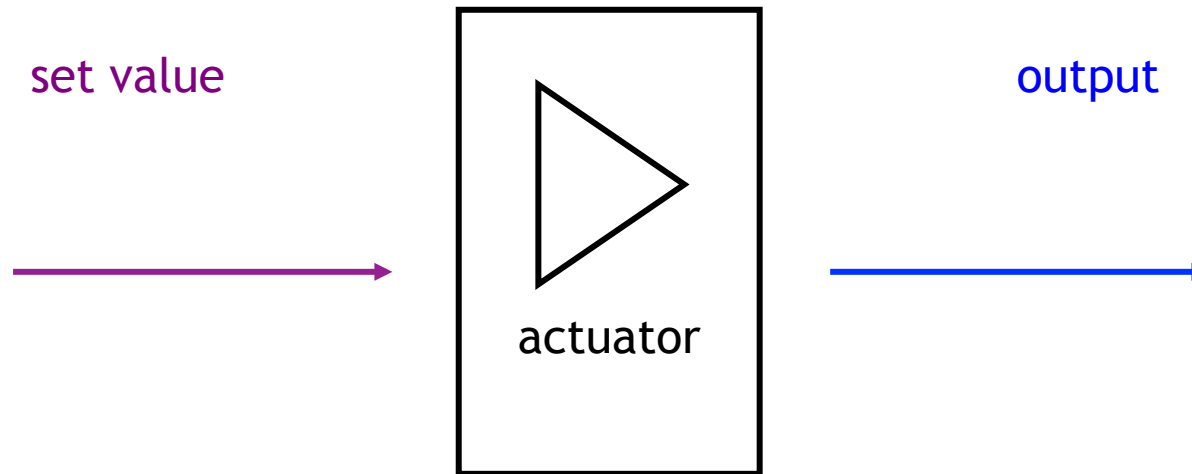


ROCO222: Intro to sensors and actuators

Lecture 1


Simple control of motor speed

Open loop control




- Set value is adjusted to specify target output
- No feedback feedforward operation
- Output is not measured and not use to change input to the plant
- There is an „open loop“

Closed loop control

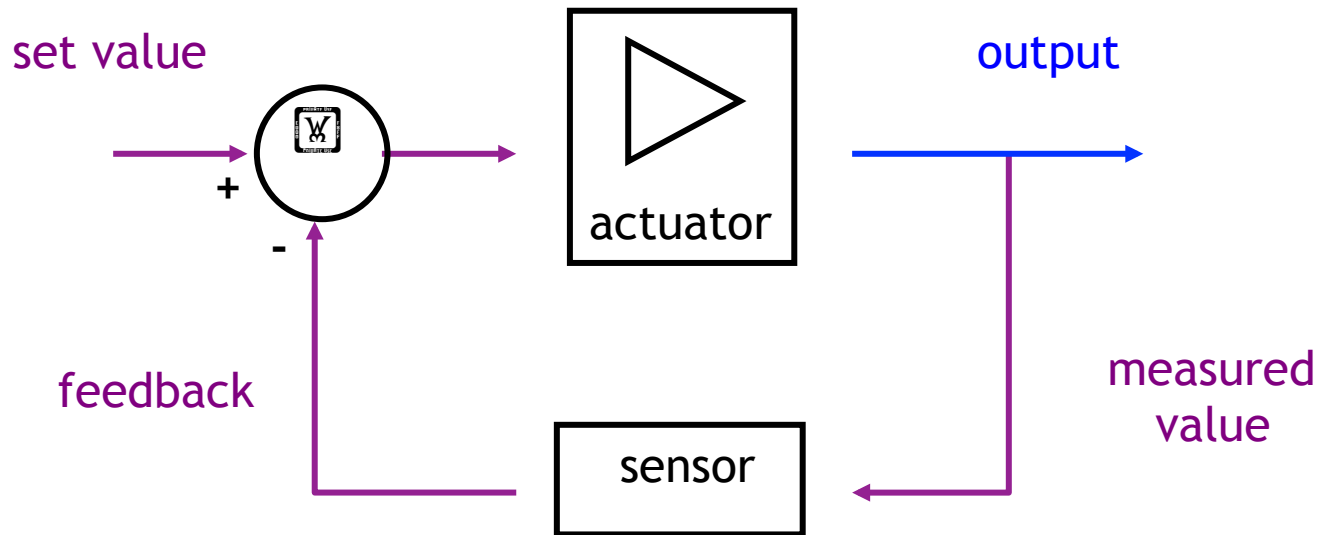

- Set value is adjusted to specify target output
- Output value is measured
- Feedback from output is used to change the input to the plant
- There is a „closed loop“


Motor operating point voltage dependent

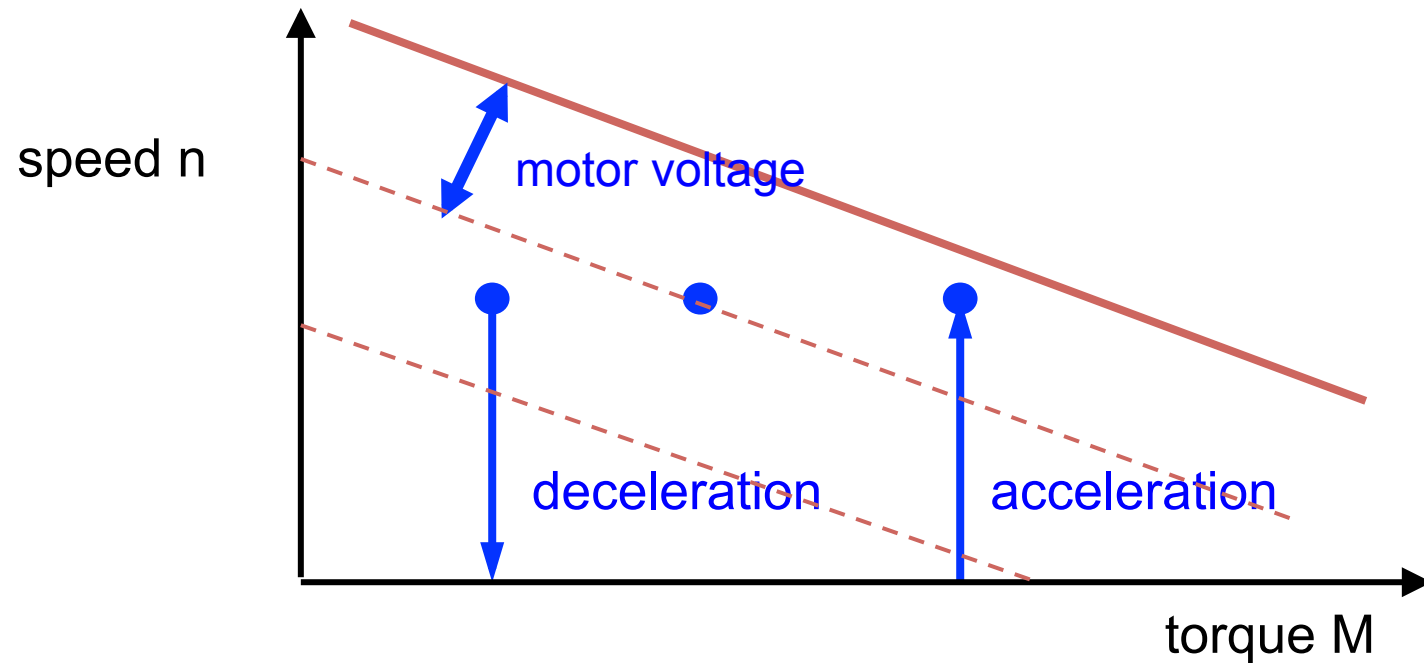

- Load operating points are characterized by a load speed n_L at a given load torque M_L
- Motor operating points lie on the speed-torque-line
- Therefore for a given load we can use motor voltage to control motor speed


Simple motor speed control

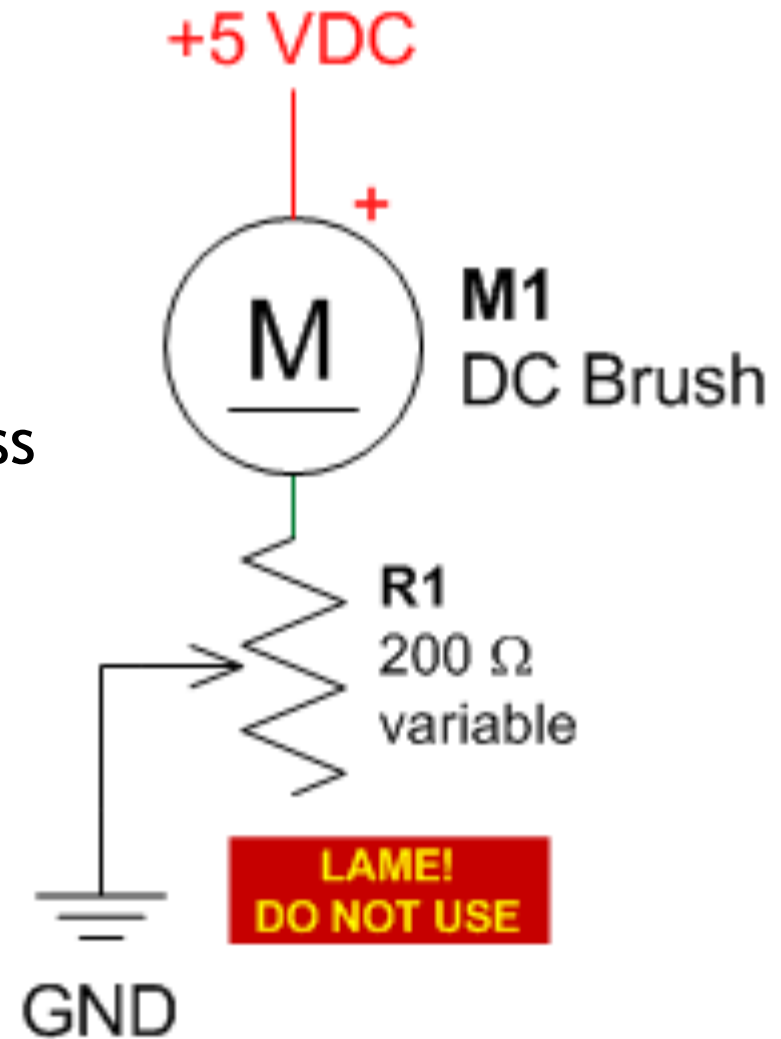- Example simple methods of motor speed control
- Using rheostat (or voltage drop across a transistor) in series with motor to limit applied voltage will realize a primitive kind of open loop control
- This will realize a primitive kind of open loop control




Linear power stage

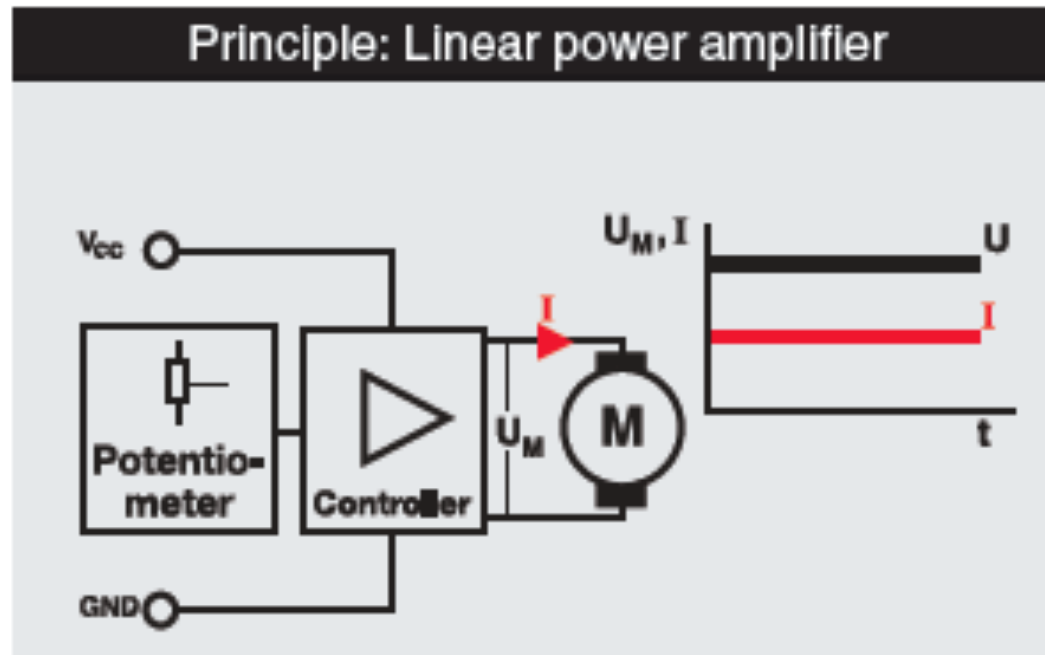- Linear power amplifier to control motor
- Operating voltage is divided between the motor and amplifier.
- Voltage drop across amplifier output stage causes power dissipation
- High currents and low motor voltages cause significant power dissipation
- Simple and favorably priced design of the power amplifier




Better motor speed control

© 2007 David Cook
www.RobotRoom.com

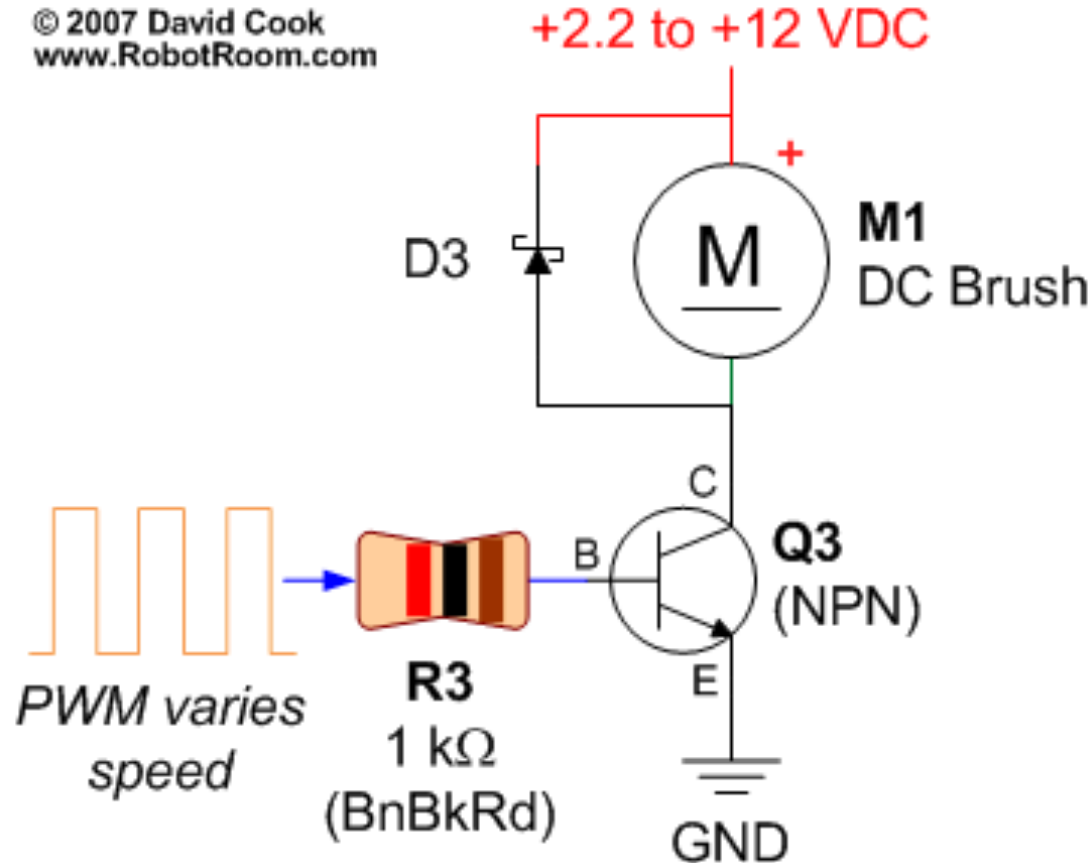

- Speed of the motor can be controlled by the duty cycle of the square wave
- Transistor either fully on or fully off
- Therefore little power dissipation in control circuitry
- This can achieve high efficiently motor control


Pulsed power stage (PWM)

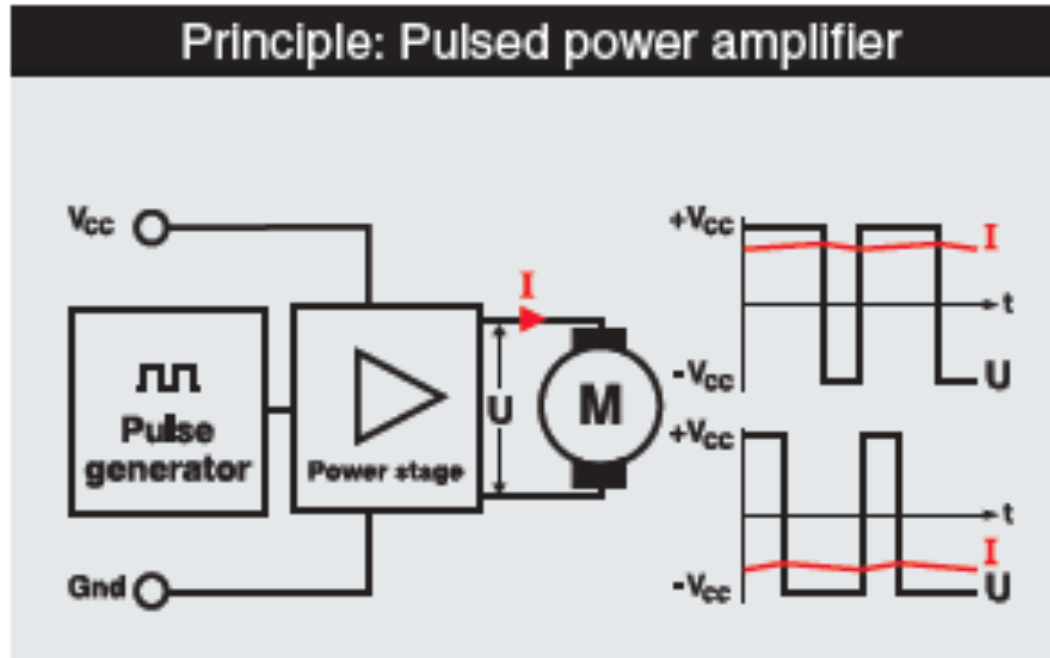

- In PWM the controller switches the motor on and off in short intervals (pulses/cycles)
- Average value of voltage changes in relation to the on-to-off time.
- If the off intervals longer, the motor drips in speed.
- Therefore little energy is converted into heat.
- Was more expensive than linear control (at least until recently)

Pulse width modulation waveforms


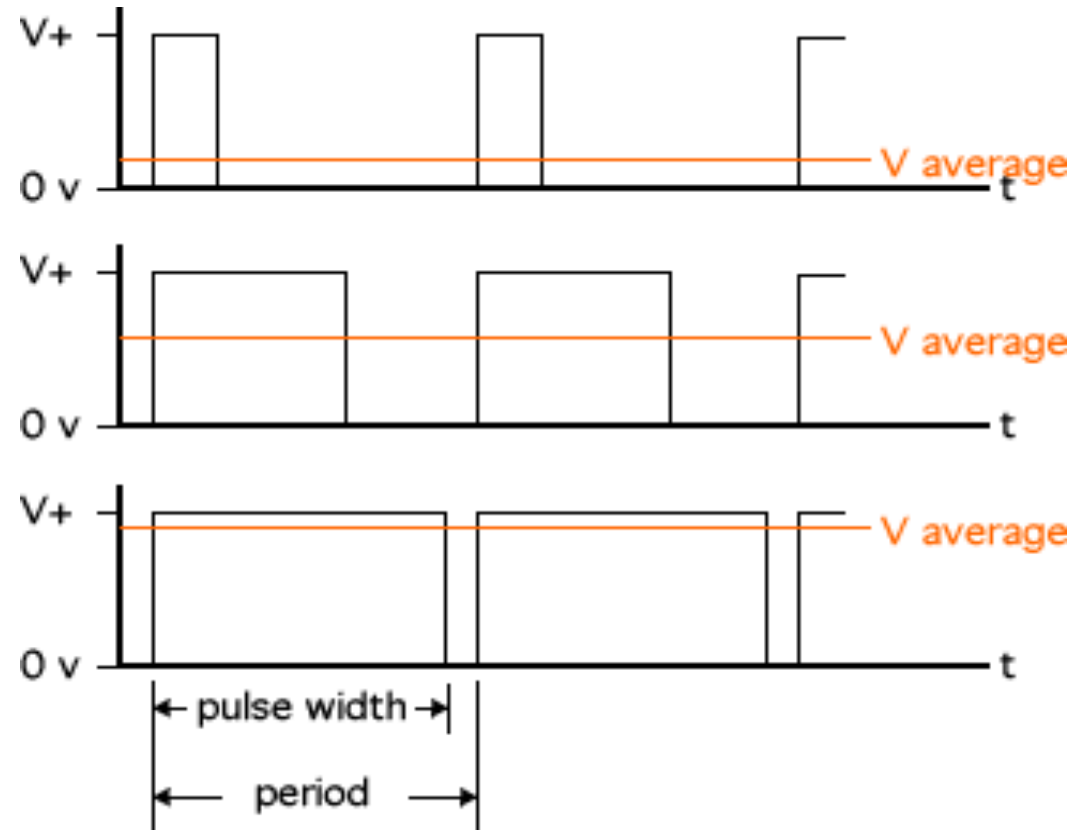
- The output of most controllers are almost entirely PWM
- Output square wave is manipulated by the controller into shorter and longer pulses
- The average of the wave gives the effective applied voltage to the motor
- This way the controller has precise control of the voltage supplied to the motor



PWM and current ripple

General ways to reduce current ripple:

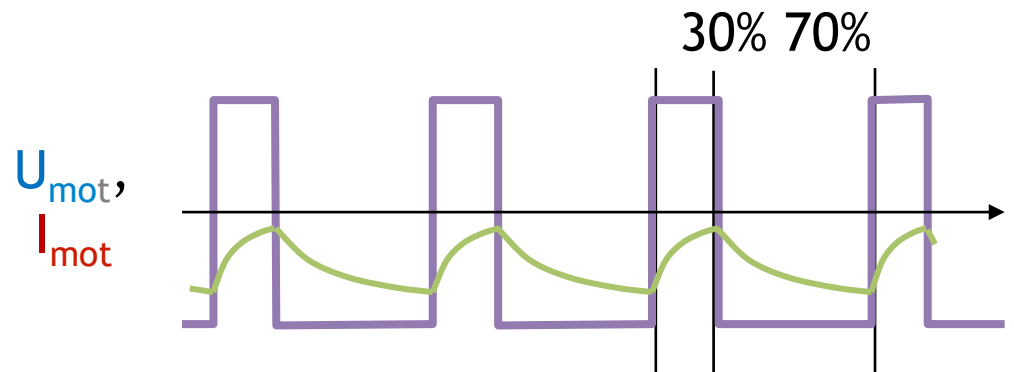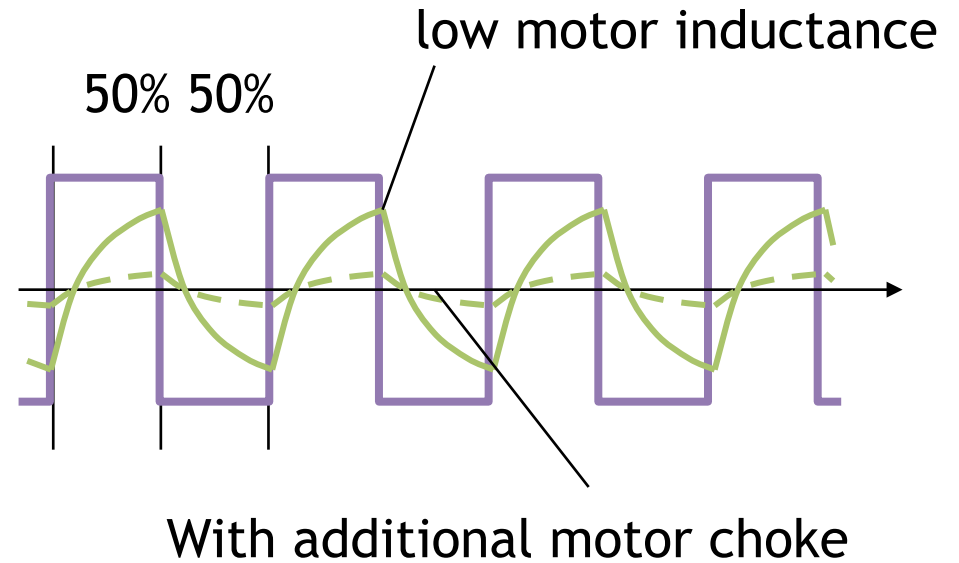- Reduce motor voltage
- Increase total inductance
- Motor choke in controller
- Additional motor choke
- Increase PWM frequency



PWM and electronic commutation

